



7447 BCD - Seven segment Display Decoder Assignment

Akkugari Ruchika
Roll No: FWC22276
akkugariruchika@gmail.com

I. ABSTRACT

This paper shows how to use the 7447 BCD-Seven segment Display Decoder to learn Boolean logic using arduino uno.

II. COMPONENTS

The required components list is given in Table: I. and seven segment display is shown in Fig.2 and IC 7447 diagram is shown in Fig.1.

Components	Value	Quantity
IC	7447	1
seven segment display		1
Arduino	UNO	1
Jumper Wires		10
Breadboard		1

TABLE I

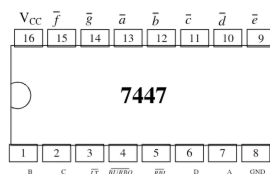


Fig. 1.

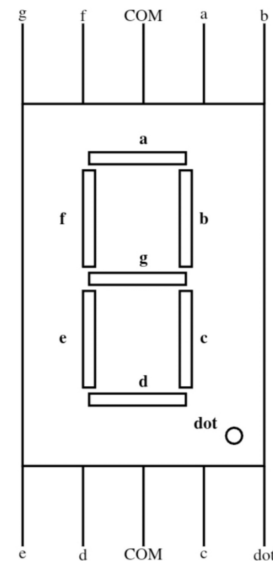


Fig. 2.

7447	\bar{a}	\bar{b}	\bar{c}	\bar{d}	\bar{e}	\bar{f}	\bar{g}
Display	a	b	c	d	e	f	g

Fig. 3.

III. PROCEDURE

- 1) Make the connections of 7447 IC and seven segment display as per below Fig.3.
- 2) Make the connections of 7447 IC and arduino uno as per below Fig.4.
- 3) Truth Table for incrementing from 0 to 9 in seven segment display

- 4) Execute the arduino code without any errors.
- 5) After upload the code into hardware setup using arduino IDE platform with hex file.

IV. RESULTS

- 1) Download the code given in the link below and execute them to see the output as shown in Fig.5.

7447	D	C	B	A
Arduino	5	4	3	2

Fig. 4.

Z	Y	X	W	D	C	B	A
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	1
0	0	1	1	0	1	0	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	1	1
0	1	1	1	1	0	0	0
1	0	0	0	1	0	0	1
1	0	0	1	0	0	0	0

TABLE II

2) <https://github.com/rajib05ra/FWC-Assignments/tree/main/Assignment>

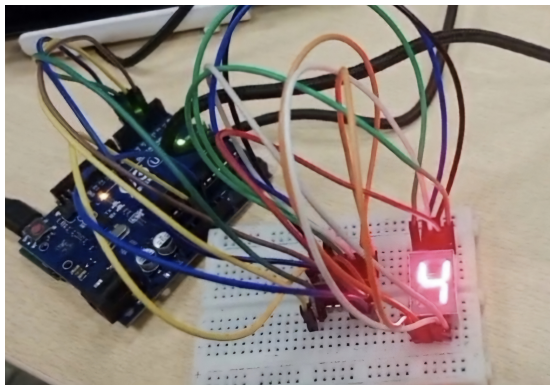


Fig. 5.

V. CONCLUSION

Hence implementation of 7447 IC, Seven segment display using arduino UNO is done.